
Digital Systems Design


Review of Combinatorial Circuit
Building Blocks:
VHDL for Combinational Circuits

Introduction to VHDL



- Designer writes a logic circuit description in VHDL source code
- VHDL compiler translates this code into a logic circuit
- Representation of digital signals in VHDL
 - Logic signals in VHDL are represented as a data object
 - VHDL includes a data type called **BIT**
 - BIT objects can assume only two values: 0 and 1

Writing simple VHDL code

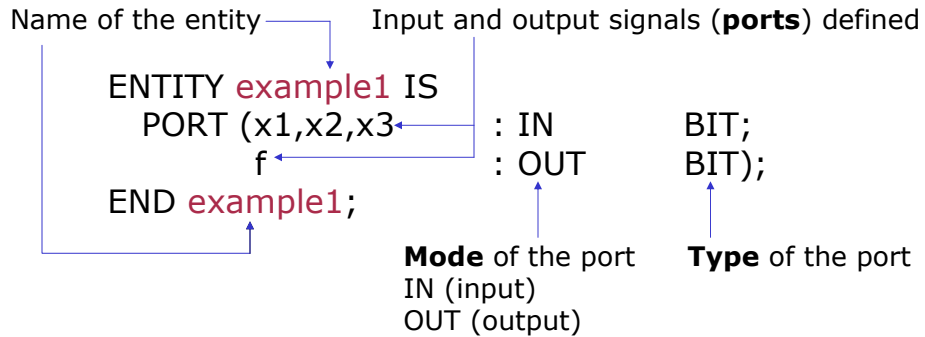- First step in writing VHDL code is to declare the input and output signals
- Done using a construct called an **entity**



Writing simple VHDL code

 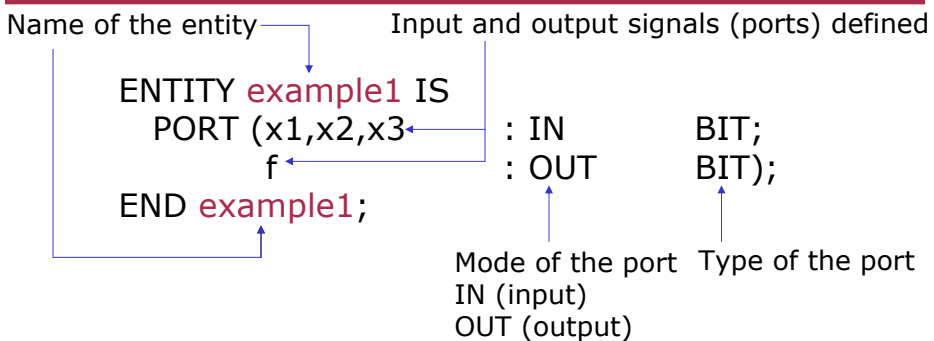

Writing simple VHDL code

- The entity specifies the inputs and outputs for a circuit, but does not describe the circuit function
- Circuit functionality is specified using a VHDL construct called an **architecture**


Architecture name →

```
ARCHITECTURE LogicFunc OF example1 IS
BEGIN
    f <= (x1 AND x2) OR (NOT x2 AND x3);
END LogicFunc;
```

Entity used by LogicFunc ↓

VHDL statement that describes the circuit functionality ↑

Complete VHDL code example

 

```
ENTITY example1 IS
    PORT (x1,x2,x3 : IN BIT;
          f       : OUT BIT);
END example1;
ARCHITECTURE LogicFunc OF example1 IS
BEGIN
    f <= (x1 AND x2) OR (NOT x2 AND x3);
END LogicFunc;
```

Boolean operators in VHDL

- VHDL has built-in support for the following operators
 - AND logical AND
 - OR logical OR
 - NOT logical NOT
 - NAND, NOR, XOR, XNOR
- Assignment operator <=
 - A variable (usually an output, mode **OUT**) should be assigned the result of the logic expression on the right hand side of the operator
- VHDL does not assume any precedence of logic operators. Use parentheses in expressions to determine precedence
- In VHDL, a logic expression is called a **simple assignment statement**. There are other types that will be introduced that are useful for more complex circuits.

Assignment statements

- VHDL provides several types of statements that can be used to assign logic values to signals
 - Simple assignment statements
 - Used previously, for logic or arithmetic expressions
 - Selected signal assignments
 - Conditional signal assignments
 - Generate statements
 - If-then-else statements
 - Case statements

Selected signal assignment

- A selected signal assignment allows a signal to be assigned one of several values, based on a selection criterion
 - Keyword **WITH** specifies that **s** is used for the selection criterion
 - Two **WHEN** clauses state that $f=w_0$ when $s=0$ and $f=w_1$ otherwise
 - The keyword **OTHERS** must be used

```
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    WITH s SELECT
        f <=    w0 WHEN '0',
              w1 WHEN OTHERS;
END Behavior;
```

Design using VHDL

- In VHDL, a logic signal is represented as a data object
 - We used a **BIT** data type before that could only take on the values 0 and 1
 - Another data type, **STD_LOGIC**, is actually preferable because it can assume several different values
 - [0, 1, Z (high impedance), - (don't care), etc]
 - The **STD_LOGIC_VECTOR** data type can be used for multi-bit values
- We must declare the library where the data type exists, and declare that we will use the data type

```
LIBRARY    ieee;
USE        ieee.std_logic_1164.all;
```

4-to-1 multiplexer VHDL code

```
LIBRARY ieee;
USE      ieee.std_logic_1164.all;
ENTITY mux4to1 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(3 DOWNTO 0);
           s      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0);
           f      : OUT     STD_LOGIC );
END mux4to1;

ARCHITECTURE Behavior OF mux4to1 IS
BEGIN
    WITH s SELECT
        f <= w(0) WHEN "00",
             w(1) WHEN "01",
             w(2) WHEN "10",
             w(3) WHEN OTHERS;
END Behavior;
```

2-to-4 binary decoder VHDL code

```
ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0);
           En     : IN      STD_LOGIC;
           y      : OUT     STD_LOGIC_VECTOR(0 TO 3));
END dec2to4;
ARCHITECTURE Behavior OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0);
BEGIN
    Enw <= En & w;           -- '&' is the VHDL concatenate operator
    WITH Enw SELECT
        y <= "1000" WHEN "100",
             "0100" WHEN "101",
             "0010" WHEN "110",
             "0001" WHEN "111",
             "0000" WHEN OTHERS;
END Behavior;
```

Conditional signal assignment

- Similar to the selected signal assignment, a **conditional signal assignment** allows a signal to be set to one of several values
 - Uses **WHEN** and **ELSE** keyword to define the condition and actions

```
ENTITY mux2to1 IS
  PORT (w0, w1, s : IN  STD_LOGIC;
        f         : OUT STD_LOGIC );
END mux2to1;
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
  f <= w0 WHEN s = '0' ELSE w1;
END Behavior;
```

Priority encoder VHDL code

```
ENTITY priority IS
  PORT ( w : IN  STD_LOGIC_VECTOR(3 DOWNTO 0);
        y : OUT STD_LOGIC_VECTOR(1 DOWNTO 0);
        z : OUT STD_LOGIC );
END priority;

ARCHITECTURE Behavior OF priority IS
BEGIN
  y <= "11" WHEN w(3) = '1' ELSE
      "10" WHEN w(2) = '1' ELSE
      "01" WHEN w(1) = '1' ELSE "00";
  z <= '0' WHEN w = "0000" ELSE '1';
END Behavior;
```

Behavioral Versus Structural VHDL

- The previous VHDL code examples are termed **behavioral** VHDL because they describe the behavior of a circuit without describing exactly how it is implemented in hardware.
- Another VHDL coding style is **structural**.
 - For structural VHDL, the user typically describes the structure of a design by interconnecting several simpler designs from a library
 - The library components may be user-defined or provided by the CAD tool vendor.

Single Bit Full Adder and Package Definition

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY fulladd IS
    PORT ( Cin, x, y      : IN    STD_LOGIC ;
          s, Cout        : OUT   STD_LOGIC ) ;
END fulladd ;

ARCHITECTURE LogicFunc OF fulladd IS
BEGIN
    s <= x XOR y XOR Cin ;
    Cout <= (x AND y) OR (Cin AND x) OR (Cin AND y) ;
END LogicFunc ;

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
PACKAGE fulladd_package IS
    COMPONENT fulladd
        PORT ( Cin, x, y : IN    STD_LOGIC ;
              s, Cout  : OUT   STD_LOGIC ) ;
    END COMPONENT ;
END fulladd_package ;
```


4-bit ripple carry adder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;
ENTITY adder4 IS
    PORT ( Cin          : IN      STD_LOGIC ;
          X, Y          : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S              : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Cout           : OUT     STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 3) ;
BEGIN
    stage0: fulladd PORT MAP ( Cin,  X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP ( C(3), X(3), Y(3), S(3), Cout ) ;
END Structure ;
```

Generate statements

- Whenever we write structural VHDL code, we often create **instances** of a particular **component**
 - A multi-stage ripple carry adder made from a number of single-bit full adders might be an example
- If we need to create a large number of instances of a component, a more compact form is desired
- VHDL provides a feature called the **FOR GENERATE** statement
 - This statement provides a loop structure for describing regularly structured hierarchical code

4-bit ripple carry adder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;
ENTITY adder4 IS
    PORT ( Cin          : IN    STD_LOGIC ;
          X, Y          : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S             : OUT   STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Cout         : OUT   STD_LOGIC ) ;
END adder4 ;
ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(0 TO 4) ;
BEGIN
    C(0) <= Cin ;
    Cout <= C(4) ;
    G1: FOR i IN 0 TO 3 GENERATE
        stages: fulladd PORT MAP (C(i), X(i), Y(i), S(i), C(i+1)) ;
    END GENERATE ;
END Structure ;
```

Process statement

- We have introduced several types of assignment statements
 - All have the property that the order in which they appear in VHDL code does not affect the meaning of the code
- Because of this property, these statements are called ***concurrent assignment statements***
- VHDL provides a second category of statements, ***sequential assignment statements***, for which the ordering of the statements may affect the meaning of the code
 - ***if-then-else*** and ***case*** statements are sequential
- VHDL requires that sequential assignment statements be placed inside another statement, the ***process*** statement

Process statement

- The process statement, or simply process, begins with the **PROCESS** keyword, followed by a parenthesized list of signals called the **sensitivity list**
 - This list includes, at most, all the signals used inside the process
 - Generally the list includes all signals that can be used to “activate” the process
- Statements inside the process are evaluated in sequential order
- Assignments made inside the process are not visible outside the process until all statements in the process have been evaluated
 - If there are multiple assignments to the same signal inside a process, only the last one has any visible effect

2-to-1 MUX as a PROCESS

ARCHITECTURE Behavior OF mux2to1 IS

BEGIN

PROCESS (w0, w1, s)

BEGIN

IF s = '0' THEN

f <= w0 ;

ELSE

f <= w1 ;

END IF ;

END PROCESS ;

END Behavior ;

**Sensitivity list,
Whenever a list entry
changes, the process
is reevaluated
(activated)**

IF-THEN-ELSE statement
to implement the MUX
function

Priority encoder (IF-THEN-ELSE)

```
ARCHITECTURE Behavior OF priority IS
BEGIN
  PROCESS ( w )
  BEGIN
    IF w(3) = '1' THEN
      y <= "11" ;
    ELSIF w(2) = '1' THEN
      y <= "10" ;
    ELSIF w(1) = '1' THEN
      y <= "01" ;
    ELSE
      y <= "00" ;
    END IF ;
  END PROCESS ;
  z <= '0' WHEN w = "0000" ELSE '1' ;
END Behavior ;
```

Priority encoder (alternative)


```
ARCHITECTURE Behavior OF priority IS
BEGIN
  PROCESS ( w )
  BEGIN
    y <= "00" ;
    IF w(1) = '1' THEN y <= "01" ; END IF ;
    IF w(2) = '1' THEN y <= "10" ; END IF ;
    IF w(3) = '1' THEN y <= "11" ; END IF ;

    z <= '1' ;
    IF w = "0000" THEN z <= '0' ; END IF ;
  END PROCESS ;
END Behavior ;
```

Implied memory in a PROCESS


ARCHITECTURE Behavior OF c1 IS
 
```
BEGIN
  PROCESS ( A, B )
  BEGIN
    AeqB <= '0';
    IF A = B THEN
      AeqB <= '1';
    END IF ;
  END PROCESS ;
END Behavior ;
```



ARCHITECTURE Behavior OF c1 IS
 
```
BEGIN
  PROCESS ( A, B )
  BEGIN
    IF A = B THEN
      AeqB <= '1';
    END IF ;
  END PROCESS ;
END Behavior ;
```



Case statement

- A **case statement** is similar to a selected assignment statement in that the case statement has a selection signal and includes WHEN clauses for various valuations of the selection signal
 - Begins with a **CASE** keyword
 - Each **WHEN** clause specifies the statements that should be evaluated when the selection signal has a specified value
 - The case statement must include a when clause for all valuations of the selection signal
 - Use the **OTHERS** keyword

2-to-1 MUX with CASE

```
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
  PROCESS ( w0, w1, s )
  BEGIN
    CASE s IS
      WHEN '0' => f <= w0 ;
      WHEN OTHERS => f <= w1 ;
    END CASE ;
  END PROCESS ;
END Behavior ;
```

2-to-4 binary decoder with CASE

```
ARCHITECTURE Behavior OF dec2to4 IS
BEGIN
  PROCESS ( w, En )
  BEGIN
    IF En = '1' THEN
      CASE w IS
        WHEN "00" => y <= "1000" ;
        WHEN "01" => y <= "0100" ;
        WHEN "10" => y <= "0010" ;
        WHEN OTHERS => y <= "0001" ;
      END CASE ;
    ELSE
      y <= "0000" ;
    END IF ;
  END PROCESS ;
END Behavior ;
```