
Digital Systems Design

Review of VHDL for Sequential Circuits

Using a D flip-flop package

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
LIBRARY altera ;  
USE altera.maxplus2.all ;
```

The dff component is only one of several built-in components for storage elements.

```
ENTITY flipflop IS  
    PORT ( D, Clock      : IN    STD_LOGIC ;  
          Resetn, Presetn : IN    STD_LOGIC ;  
          Q               : OUT   STD_LOGIC ) ;  
END flipflop ;
```

```
ARCHITECTURE Structure OF flipflop IS  
BEGIN  
    dff_instance: dff PORT MAP ( D, Clock, Resetn, Presetn, Q ) ;  
END Structure ;
```

Resetn and Presetn: Active low signals

Code for a gated D latch

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY latch IS
    PORT (    D, Clk : IN    STD_LOGIC ;
           Q       : OUT   STD_LOGIC);
END latch ;

ARCHITECTURE Behavior OF latch IS
BEGIN
    PROCESS ( D, Clk )
    BEGIN
        IF Clk = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

USES IMPLIED MEMORY

Code for a D flip-flop

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT (    D, Clock      : IN    STD_LOGIC ;
           Q               : OUT   STD_LOGIC);
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

POSITIVE EDGE TRIGGERED

Code for a D flip-flop (alternate)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
  PORT ( D, Clock      : IN  STD_LOGIC ;
        Q              : OUT STD_LOGIC );
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
  PROCESS ( Clock )
  BEGIN
    IF RISING_EDGE(Clock) THEN
      Q <= D ;
    END IF ;
  END PROCESS ;
END Behavior ;
```

**POSITIVE EDGE TRIGGERED. USE
FALLING_EDGE FOR NEGATIVE EDGE**

Code for a D flip-flop (alternate)

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY flipflop IS
  PORT ( D, Clock      : IN  STD_LOGIC ;
        Q              : OUT STD_LOGIC );
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
  PROCESS
  BEGIN
    WAIT UNTIL Clock'EVENT AND Clock = '1' ;
    Q <= D ;
  END PROCESS ;
END Behavior ;
```

POSITIVE EDGE TRIGGERED

D flip-flop with synchronous reset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
  PORT (      D, Resetn, Clock      : IN   STD_LOGIC ;
         Q                                           : OUT  STD_LOGIC);
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
  PROCESS
  BEGIN
    WAIT UNTIL Clock'EVENT AND Clock = '1' ;
    IF Resetn = '0' THEN
      Q <= '0' ;
    ELSE
      Q <= D ;
    END IF ;
  END PROCESS ;
END Behavior ;
```

D flip-flop with MUX input

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY muxdff IS
  PORT (      D0, D1, Sel, Clock      : IN   STD_LOGIC ;
         Q                                           : OUT  STD_LOGIC);
END muxdff ;

ARCHITECTURE Behavior OF muxdff IS
BEGIN
  PROCESS
  BEGIN
    WAIT UNTIL Clock'EVENT AND Clock = '1' ;
    IF Sel = '0' THEN
      Q <= D0 ;
    ELSE
      Q <= D1 ;
    END IF ;
  END PROCESS ;
END Behavior ;
```

D flip-flop with enable input

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( enable, d, clk      : IN   STD_LOGIC ;
          q                    : OUT  STD_LOGIC ) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS(clk)
    BEGIN
        IF enable='0' THEN null;
        ELSIF RISING_EDGE(clk) THEN
            q <= d;
        END IF;
    END PROCESS ;
END Behavior ;
```

This will be our preferred method for creating a D flip-flop or a multibit register with enable.

D flip-flop with asynchronous reset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( reset_n, d, clk    : IN   STD_LOGIC ;
          q                   : OUT  STD_LOGIC ) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS(clk,reset_n)
    BEGIN
        IF reset_n='0' THEN
            q <= '0';
        ELSIF RISING_EDGE(clk) THEN
            q <= d;
        END IF;
    END PROCESS ;
END Behavior ;
```

This will be our preferred method for creating a D flip-flop or a multibit register with reset.


Arbitrary FSM design using CAD tools

- VHDL provides a number of constructs for designing finite state machines
- There is not a standard way for defining an FSM
- Basic approach
 - Create a user-defined data type to represent the possible states of an FSM
 - This signal represents the outputs (state variables) of the flip-flops that implement the states in the FSM
 - VHDL compiler chooses the appropriate number of flip-flops during the synthesis process
 - The state assignment can be done by the compiler or can be user specified

User defined data types

- The **TYPE** keyword will be used to define a new data type used to represent states in the FSM

TYPE State_type IS (A, B, C);

 

Defines a data type (called State_type) that can take on three distinct values: A, B, or C.

Representing states


- A **SIGNAL** is defined, of the user-defined **State_type**, to represent the flip-flop outputs

```
TYPE State_type IS (A, B, C);  
SIGNAL y: State_type;
```

The signal, y , can be used to represent the flip-flop outputs for an FSM that has three states

Design example

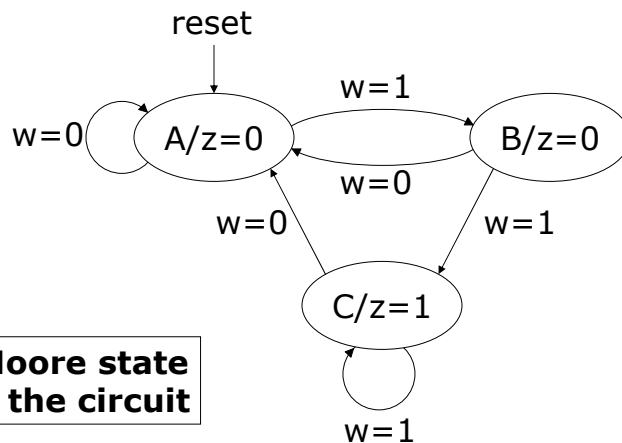- Create a VHDL description for a circuit that detects a '11' input sequence on an input, w



Recall the Moore state diagram for the circuit

VHDL design example

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY detect IS
    PORT(      clk, resetn, w   : IN   STD_LOGIC ;
           z           : OUT  STD_LOGIC);
END detect ;

ARCHITECTURE Behavior OF detect IS
    TYPE State_type IS (A,B,C) ;
    SIGNAL y: State_type ;
BEGIN
```

VHDL design example continued

```
PROCESS ( resetn, clk )
BEGIN
    IF resetn = '0' THEN
        y <= A;
    ELSIF RISING_EDGE(clk) THEN
        CASE y IS
            WHEN A =>
                IF w='0' THEN
                    y <= A;
                ELSE
                    y <= B;
                END IF;
            WHEN B =>
                IF w='0' THEN
                    y <= A;
                ELSE
                    y <= C;
                END IF;
        END CASE;
    END IF;
END PROCESS
z <= '1' WHEN y=C ELSE '0';
END Behavior;
```


Alternative style of VHDL code

- Another form for describing the circuit in VHDL is to define two signals to represent the state of the FSM
 - One signal, **y_present**, defines the present state of the FSM
 - The second, **y_next**, defines the next state of the machine
- This notation uses **y** (present state) and **Y** (next state) for state information
- Two PROCESS statements will be used to describe the machine
 - The first describes the STATE TABLE as a combinational circuit
 - The second describes the flip-flops, stating that **y_present** should take on the value of **y_next** after each positive clock edge

Alternate VHDL description

```
ARCHITECTURE Behavior OF detect IS
  TYPE State_type IS (A,B,C);
  SIGNAL y_present, y_next: State_type;
BEGIN
PROCESS(w,y_present)
BEGIN
  CASE y_present IS
    WHEN A =>
      IF w='0' THEN
        y_next <= A;
      ELSE
        y_next <= B;
      WHEN B =>
        IF w='0' THEN
          y_next <= A;
        ELSE
          y_next <= C;
        WHEN C =>
          IF w='0' THEN
            y_next <= A;
          ELSE
            y_next <= C;
          WHEN C =>
            IF w='0' THEN
              y_next <= A;
            ELSE
              y_next <= C;
            END CASE;
          END PROCESS;
        PROCESS(clk,resetn)
        BEGIN
          IF resetn='0' THEN
            y_present <= A;
          ELSIF RISING_EDGE(clk) THEN
            y_present <= y_next;
          END IF;
        END PROCESS
        z <= '1' WHEN y_present=C ELSE '0';
      END Behavior;
```

Specifying a state assignment

- With the previous designs, state assignment is done by the VHDL compiler
- State assignments can be user specified using the following constructs


```
ARCHITECTURE Behavior OF simple IS
  TYPE State_type IS (A, B, C);
  ATTRIBUTE ENUM_ENCODING           : STRING;
  ATTRIBUTE ENUM_ENCODING OF State_type : TYPE IS "00 01 11";
  SIGNAL y_present, y_next : State_type;
BEGIN
```

Or

```
ARCHITECTURE Behavior OF simple IS
  SIGNAL y_present, y_next : STD_LOGIC_VECTOR(1 DOWNTO 0);
  CONSTANT A : STD_LOGIC_VECTOR(1 DOWNTO 0) := "00";
  CONSTANT B : STD_LOGIC_VECTOR(1 DOWNTO 0) := "01";
  CONSTANT C : STD_LOGIC_VECTOR(1 DOWNTO 0) := "11";
```

VHDL code of a Mealy FSM

 - A Mealy FSM can be described in a similar manner as a Moore FSM
- The state transitions are described in the same way as the original VHDL example
- The major difference in the case of a Mealy FSM is the way in which the code for the output is written
- Recall the Mealy state diagram for the '11' sequence detector



Mealy '11' detector VHDL code

```
ARCHITECTURE Behavior OF detect IS
    TYPE State_type IS (A,B) ;
    SIGNAL y: State_type ;
BEGIN
    PROCESS(resetn,clk)
    BEGIN
        IF resetn='0' THEN
            y <= A;
        ELSEIF RISING_EDGE(clk) THEN
            CASE y IS
                WHEN A =>
                    IF w='0' THEN y<= A;
                    ELSE y<= B;
                    END IF;
                WHEN B =>
                    IF w='0' THEN y<= A;
                    ELSE y<= B;
                    END IF;
            END CASE;
        END IF;
    END PROCESS;
    PROCESS(y,w)
    BEGIN
        CASE y IS
            WHEN A =>
                z <='0';
            WHEN B =>
                z <= w;
            END CASE;
        END PROCESS;
    END Behavior;
```