

ELE 373: Advanced Digital Architecture and Design

February 26, 2009

Project 1.

Design and test an n-bit parallel two's complement adder using only concurrent VHDL code. Your target device is a GAL 22V10. Build the largest adder that will fit into your target device. Include an overflow detection circuit as part of your design.